



Gisselquist
Technology, LLC

2. Registers

Daniel E. Gisselquist, Ph.D.





Lesson Overview



▷ Lesson Overview

Registers

Combinatorial

Latches

Flip Flops

Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

PPS-I

PPS-II

Stretch

Too Slow

Dimmer

Exercises

- What is a register (**reg**)?
- How do things change with time?
- Discover the system clock

Objectives

- Learn how to create combinatorial logic with registers
- Learn to create clocked (synchronous) logic
- Understand that registers can “remember” things
- Understand where your System Clock comes from
- Timing Checks, and why they are important



Registers



Lesson Overview

▷ Registers

Combinatorial

Latches

Flip Flops

Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

PPS-I

PPS-II

Stretch

Too Slow

Dimmer

Exercises

Why use registers?

- Wires have no memory
- Only registers can hold state (data)

Two basic types, both set with an **always**

1. Combinatorial: Like wires

```
always @(*)  
    A = B;
```


This form can be easier to read when the logic becomes complex

2. Synchronous: Only changes values on a clock

```
always @(posedge i_clk)  
    A <= B;
```



Combinatorial Regs

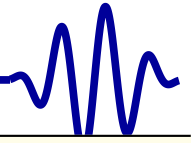

- Lesson Overview
- Registers
 - ▷ Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises


```
always @(*)
    A = 9'h87;
```

- Registers can only be assigned in **always** blocks.
- Always blocks may consist of one statement, or
- Many statements between a **begin** and **end** pair

```
always @(*)
begin
    o_led = A ^ i_sw;
    o_led = o_led + 7;
    if (i_reset)
        o_led = 0;
end
```



Combinatorial Regs

 

- Lesson Overview
- Registers
 - ▷ Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

```
always @(*)
begin
    o_led = A ^ i_sw;
    o_led = o_led + 7;
    if (i_reset)
        o_led = 0;
end
```

This block

- Looks like software
 - Acts like you would expect in a simulator
 - Takes no time at all in hardware
- The hardware acts as if all statements were done at once

Only use “=” in a combinatorial always block



Latches



What happens here?

```
input    wire    i_S;
input    wire    [7:0] i_V;
output   reg     [7:0] o_R;

always @(*)
  if (i_S)
    o_R = i_V;
```

This is called a latch

- It requires memory
- May do one thing in simulation, another in hardware
- Most FPGA's don't support latches
- Can have subtle timing problems in hardware

Avoid using latches!

- Lesson Overview
- Registers
- Combinatorial
- ▷ Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Last Assignment Wins



What happens here?

```
always @(*)
begin
    o_R = 0;
    if (i_S)
        o_R = i_V;
end
```


No latch is inferred

- This is a very useful pattern!
- o_R now has a default value
This prevents a latch from being inferred
- No memory is required
- The last assignment gives o_R its final value

- Lesson Overview
- Registers
- Combinatorial
 - ▷ Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Flip Flops

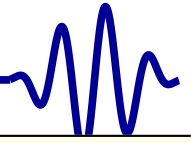

- Lesson Overview
- Registers
- Combinatorial
- Latches
- ▷ Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises


```
reg      [9:0]  A;

always  @(posedge i_clk)
        A <= A + 1'b1;
```

- Any registers set within an **always** @(posedge i_clk) block will transition to their new values on the next clock edge only
 - *Only a bonafide clock edge should be used*
 - Do not transition on anything you create in logic
- Note that we are using <= for assignment
 - This is a *non-blocking* assignment
 - Most, if not all, clocked register should be set with <=



Blocking

 

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- ▷ Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

- This is a non-blocking assignment

```
always @(posedge i_clk)
    A <= A + 1'b1;
```

- Blocking assignment

```
always @(posedge i_clk)
    A = A + 1'b1;
```

- A blocking assignment's value may be referenced again before the clock edge
 - Creates the appearance of time passing within the block
 - *It may also cause simulation-hardware mismatch*
 - *Use with caution*
- In this case, both generate the same logic



Non-Blocking



Lesson Overview

Registers

Combinatorial

Latches

Flip Flops

▷ Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

PPS-I

PPS-II

Stretch

Too Slow

Dimmer

Exercises

What value will be given for A?

- Assume it starts at zero
- What will it be after one clock tick?

```
always @(posedge i_clk)
begin
    A <= 5;
    A <= A + 1'b1;
end
```

- The assignment only takes place on the clock edge
- Last assignment wins
- A is set to 1, then 2 on the next clock, 3 on the clock after, etc.



Blocking



Lesson Overview

Registers

Combinatorial

Latches

Flip Flops

▷ Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

PPS-I

PPS-II

Stretch

Too Slow

Dimmer

Exercises

Now what value will be given for A?


- Assume it starts at zero
- What will it be after one clock tick?

```
always @(posedge i_clk)
begin
    A = 5;
    A = A + 1'b1;
end
```

- Again, the assignment only takes place on the clock edge
- It appears as though it took several steps
- A is set to 6



Blocking

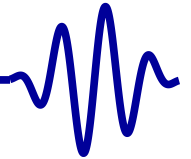

What if something depends upon A in another block?

- Assume A=0 before the clock tick

```
always @(posedge i_clk)
begin
    A = 5;
    A = A + 1'b1;
end

always @(posedge i_clk)
    B <= A;
```

- This result is *simulation dependent!*
- B may be set to 0, or it may be set to 6

Don't do this! Use <= within an **always** @(posedge i_clk)

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- ▷ Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Non-Blocking



Now what will B be set to?

- Assume A=0 before the clock tick

```
always @(posedge i_clk)
begin
    A <= 5; // Ignored!
    A <= A + 1'b1;
end

always @(posedge i_clk)
    B <= A;
```

- A will be set to 1, and B will be set to 0
- On the next clock, A will be set to 2 and B to 1, etc.

Now simulation matches hardware



All in Parallel



- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- ▷ All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

- A design may contain multiple always blocks
- The hardware will execute all at once
- The simulator will execute one at a time

Rules: When using the simulator, ...

- Make sure your design can be synthesized
- Make sure it fits within your chosen device
 - This is not a simulator task
 - Requires using the synthesizer periodically
- Make sure it maintains an appropriate clock rate
 - We'll get to timing checks in a moment



Feedback



- Wires in a loop created circular logic
- Clocked registers in a loop creates feedback

```
assign    err = i_actual - o_command;  
always @(posedge i_clk)  
begin  
           o_command<=o_command+(err >> 5);  
end
```

Feedback is used commonly in control systems

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- ▷ Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Blinky



Lesson Overview

Registers

Combinatorial

Latches

Flip Flops

Blocking

All in Parallel

Feedback

▷ Blinky

Broken Blinky

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

PPS-I

PPS-II

Stretch

Too Slow

Dimmer

Exercises

Let's make an LED blink!

```
module blinky(i_clk, o_led);
    input    wire    i_clk;
    output   wire    o_led;

    reg      [26:0]   counter;
    initial counter = 0;
    always @(posedge i_clk)
        counter <= counter + 1'b1;

    assign   o_led = counter[26];
endmodule
```

Feel free to synthesize and try this

- The LED should blink at a steady rate
- Rate is determined by the 26 above



Broken Blinky



- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
 - ▷ Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

Here's a common beginner mistake

```
reg    counter;  
  
always @(posedge i_clk)  
    counter <= counter + 1'b1;  
  
assign o_led = counter;
```

Don't make this mistake

- Notice that counter is only 1-bit
- This will blink at half the `i_clk` frequency
- Result is typically way too fast to see any changes
- LED may glow dimly
- Need to slow it down



Verilator



- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- ▷ Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

Simulating our design (blinky) now requires a clock:

```
void    tick (Vblinky *tb) {  
    // The following eval() looks  
    // redundant ... many of hours  
    // of debugging reveal its not  
    tb->eval();  
    tb->i_clk = 1;  
    tb->eval();  
    tb->i_clk = 0;  
    tb->eval();  
}
```

- We'll need to toggle the clock input for anything to happen
- This operation is so common, it deserves its own function, **tick()**



Verilator



We can now simplify our main loop a touch

```
int main(int argc, char **argv) {
    int last_led;
    // .... Setup

    last_led = tb->o_led;
    for(int k=0; k<(1<<20); k++) {
        // Toggle the clock
        tick(tb);

        // Now let's print the LEDs value
        // anytime it changes
        if (last_led != tb->o_led) {
            printf("k_=%7d, ", k);
            printf("led_=%d\n", tb->o_led);
        } last_led = tb->o_led;
    }
}
```

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- ▷ Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Verilator



Lesson Overview

Registers

Combinatorial

Latches

Flip Flops

Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

▷ Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

PPS-I

PPS-II

Stretch

Too Slow

Dimmer

Exercises

Can we simulate this? Not easily

- Counting to 2^{27} may take seconds in hardware, but ...
- It's extreme slow in simulation.
- Let's speed blinky up—just for simulation
- We can do this by adjusting the width of the counter

We'll use a parameter to do this

```
parameter          WIDTH=27;
reg                [WIDTH-1:0]    counter;
// .....
assign             o_led = counter[WIDTH-1];
```



Parameters



- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
 - ▷ Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

Parameters are very powerful! They allow us to


- Reconfigure a design, after it's been written
- Examples:
 - ZipCPU cache sizes can be adjusted by parameters
 - Internal memory sizes, implement the divide instruction or not, specify the type of multiply
 - Default serial port speed, number of GPIO pins supported by a GPIO controller, and more

Verilator argument `-GWIDTH=12` sets the `WIDTH` parameter to 12

```
% verilator -Wall -GWIDTH=12 -cc blinky.v
```



Sim Result

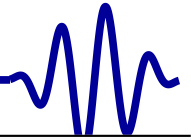


- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- ▷ Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

```
% ./blinky
k =      2047 , led = 1
k =     4095 , led = 0
k =     6143 , led = 1
k =     8191 , led = 0
k =    10239 , led = 1
k =    12287 , led = 0
k =    14335 , led = 1
k =    16383 , led = 0
k =    18431 , led = 1
k =    20479 , led = 0
# .... (Lines skipped for brevity)
%
```



Trace Generation

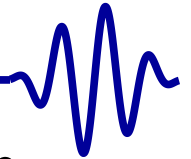

This is easy. For more complex designs, we'll need a trace

- That means writing to a trace file on every clock

Steps

1. Add the `--trace` option to the Verilator command line

```
% verilator -Wall --trace -GWIDTH=12 \  
    -cc blinky.v
```

2. Create a trace from your `.cpp` file

```
#include "verilated_vcd_c.h"  
// ...  
int main(int argc, char **argv) {  
    // ...  
    unsigned tickcount = 0;  
    // ...  
}
```

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
 - Trace
 - ▷ Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Trace Generation



- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
 - Trace
 - ▷ Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

Create the trace file within C++

```
// ...
int main(int argc, char **argv) {
    // ...
    // Generate a trace
    Verilated::traceEverOn(true);
    VerilatedVcdC* tfp = new VerilatedVcdC;
    tb->trace(tfp, 99);
    tfp->open("blinkytrace.vcd");

    // ...
    for(int k=0; k<(1<<20); k++) {
        tick(++tickcount, tb, tfp);
        // ...
    }
}
```




Trace Generation




3. Write trace data on every clock

```
void    tick(int tickcount , Vblinky *tb ,  
          VerilatedVcdC* tfp) {  
    tb->eval();  
    if (tfp) // dump 2ns before the tick  
        tfp->dump(tickcount * 10 - 2);  
    tb->i_clk = 1;  
    tb->eval();  
    if (tfp) // Tick every 10ns  
        tfp->dump(tickcount * 10);  
    tb->i_clk = 0;  
    tb->eval();  
    if (tfp) { // Trailing edge dump  
        tfp->dump(tickcount * 10 + 5);  
        tfp->flush();  
    }  
}
```

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
 - Trace
 - ▷ Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Trace Generation

 

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
 - Trace
 - ▷ Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

- You'll need to add `verilated_vcd_c.cpp` to your `g++` build command in order to support generating a trace as well

```
% export VINC=/usr/share/verilator/include
% g++ -I${VINC} -I obj_dir
      ${VINC}/verilated.cpp
      ${VINC}/verilated_vcd_c.cpp blinky.cpp
      obj_dir/Vblinky_ALL.a -o blinky
```

- Now, running `blinky` will generate a trace


```
% ./blinky
# ...
```

- You can view it with `GTKwave`


```
% gtkwave blinkytrace.vcd
```



GTKWave

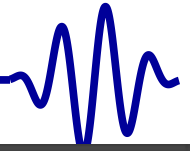

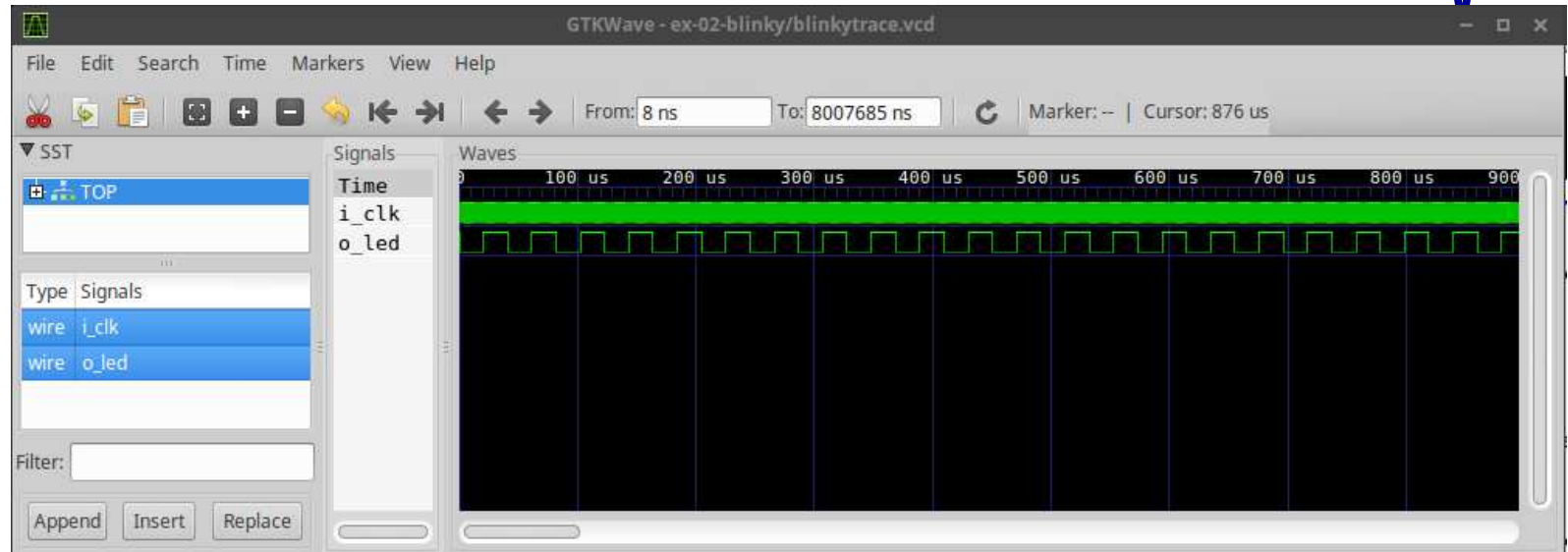- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
 - ▷ GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



This is how logic debugging is done

- The simulator trace shows you every register's value
- ... at every clock tick
- You can zoom in to find any bugs



Strobe



How is this design different from blinky?

```
module strobe(i_clk, o_led);  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    reg      [26:0]   counter;  
  
    always @(posedge i_clk)  
            counter <= counter + 1'b1;  
  
    assign   o_led = &counter[26:24];  
endmodule
```

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- ▷ Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises



Lesson Overview

Registers

Combinatorial

Latches

Flip Flops

Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

▷ PPS-I

PPS-II

Stretch

Too Slow

Dimmer


Exercises

Can we get an LED to blink once per second?

```
always @(posedge i_clk)
  if (counter >= CLOCK_RATE_HZ/2-1)
  begin
    counter <= 0;
    o_led <= !o_led;
  end else
    counter <= counter + 1;
```


When $CLOCK_RATE_HZ/2$ ticks have passed, the LED will toggle

 - This structure is known as an integer clock divider
- It offers an exact division



Can we get an LED to blink once per second?
 
```
parameter CLOCK_RATE_HZ = 100_000_000;  
parameter [31:0] INCREMENT  
            = (1<<30)/(CLOCK_RATE_HZ / 4);  
input    wire    i_clk;  
output  wire    o_led;  
  
reg     [31:0]  counter;  
  
initial counter = 0;  
always @(posedge i_clk)  
        counter <= counter + INCREMENT;  
  
assign  o_led = counter[31];
```



- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- ▷ PPS-II
- Stretch
- Too Slow
- Dimmer
- Exercises

```

parameter CLOCK_RATE_HZ = 100_000_000;
parameter [31:0] INCREMENT
            = (1<<30)/(CLOCK_RATE_HZ / 4);
always @(posedge i_clk)
        counter <= counter + INCREMENT;
    
```


- After CLOCK_RATE_HZ clock edges, the counter will roll over
- The divide by four above, on both numerator and denominator, is just to keep this within 32-bit arithmetic

$$\text{INCREMENT} = \frac{2^{32}}{\text{CLOCK_RATE_HZ}}$$

- This is called a *fractional clock divider*
 - The division isn't exact
 - It's often good enough



Stretch

 


- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- ▷ Stretch
- Too Slow
- Dimmer
- Exercises

```
module stretch(i_clk, i_event, o_led);  
    input    wire    i_clk, i_event;  
    output   wire    o_led;  
  
    reg      [26:0]   counter;  
  
    always @(posedge i_clk)  
    if (i_event)  
        counter <= 0;  
    else if (!counter[26])  
        counter <= counter + 1;  
  
    assign   o_led = !counter[26];  
endmodule
```

FPGA signals are often too fast to see



Stretch

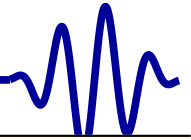

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- ▷ Stretch
- Too Slow
- Dimmer
- Exercises


```
module stretch(i_clk, i_event, o_led);  
    // ...  
    reg [26:0] counter;  
    always @(posedge i_clk)  
    if (i_event)  
        counter <= 0;  
    else if (!counter[26])  
        counter <= counter + 1;  
    assign o_led = !counter[26];  
endmodule
```

FPGA signals are often too fast to see

- This slows them down to eye speed
- Only works for a single event though
- Multiple events would overlap, and be no longer distinct



Too Slow

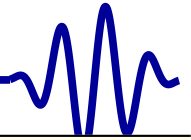

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- ▷ Too Slow
- Dimmer
- Exercises

```
module tooslow(i_clk, o_led);  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    parameter                                NBITS = 1024;  
    reg      [NBITS-1:0]    counter;  
  
    always @(posedge i_clk)  
        counter <= counter + 1;  
  
    assign  o_led = counter[NBITS-1];  
endmodule
```

This is guaranteed to fail a timing check

- It's now time to learn how to check timing
- This design should fail, for reasonable clock speeds



Too Slow



- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- ▷ Too Slow
- Dimmer
- Exercises

Follow your chip vendor's instructions to do a timing check

- Use your system clock frequency
 - For now, that's the clock frequency coming into your board
 - We'll adjust it later
- Make sure this design fails
 - The carry chain takes time to propagate
 - Extra long carry chains take extra long
 - If the propagation doesn't complete before the next clock ... your design will fail (like this one)
- From now on, *always* check timing for a design
 - Before loading it onto a board
 - Every now and then while simulating



Dimmer



Can you tell me what this will do?

```
module dimmer(i_clk, o_led);  
    input    wire    i_clk;  
    output  wire    o_led;  
  
    reg      [27:0]  counter;  
  
    always @(posedge i_clk)  
        counter <= counter + 1;  
  
    assign  o_led = (counter [7:0]  
                    < counter [27:20]);  
endmodule
```

- Lesson Overview
- Registers
- Combinatorial
- Latches
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- PPS-I
- PPS-II
- Stretch
- Too Slow
- ▷ Dimmer
- Exercises



Exercises



Lesson Overview

Registers

Combinatorial

Latches

Flip Flops

Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

PPS-I

PPS-II

Stretch

Too Slow

Dimmer

▷ Exercises

- Implement blinky on your hardware
- Implement one of the two PPS designs
 - Using a stopwatch, verify the blink rate of 1Hz
 - Make the blinks shorter, but at the same frequency
- Verify that the 1024 bit `tooslow` counter will fail timing
- Implement the dimmer